
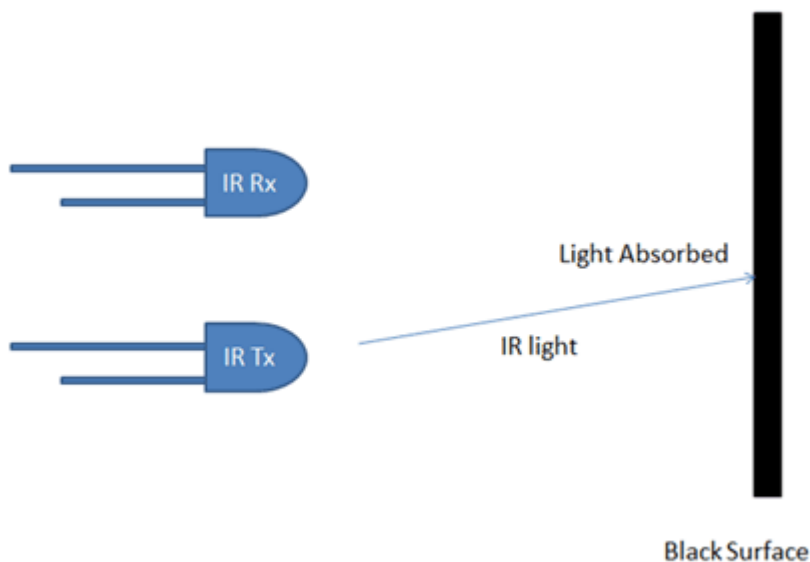


Concepts of Line Follower

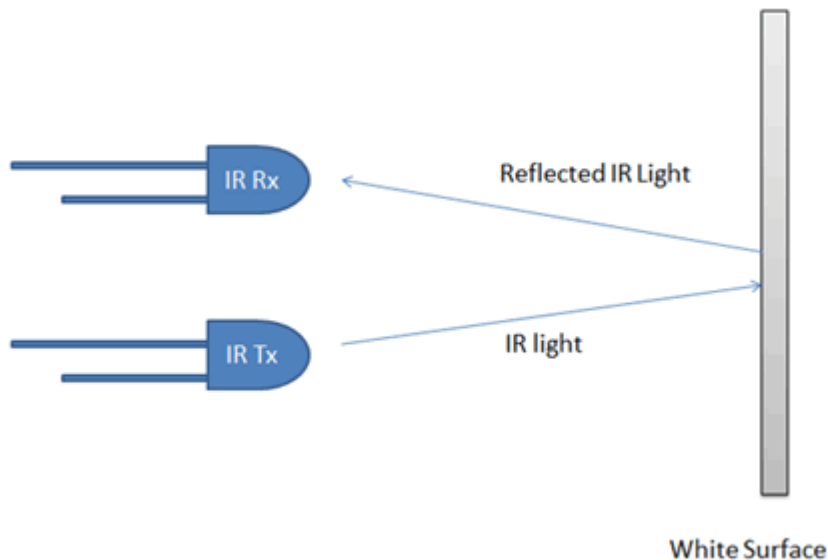Concept of working of line follower is related to light. We use here the behavior of light at black and white surface. When light fall on a white surface it is almost full reflected and in case of black surface light is completely absorbed. This behavior of light is used in **building a line follower robot**.



In this **arduino based line follower robot** we have used IR Transmitters and IR receivers also called photo diodes. They are used for sending and receiving light. IR transmits infrared lights. When infrared rays falls on white surface, it's reflected back and caught by photodiodes which generates some voltage changes. When IR light falls on a black surface, light is absorb by the black surface and no rays are reflected back, thus photo diode does not receive any light or rays.

Here in this arduino line follower robot when sensor senses white surface then arduino gets 1 as input and when senses black line arduino gets 0 as input.

Circuit Explanation

The whole **arduino line follower robot** can be divided into 3 sections: sensor section, control section and driver section.

Sensor section:

This section contains IR diodes, potentiometer, Comparator (Op-Amp) and LED's. Potentiometer is used for setting reference voltage at comparator's one terminal and IR sensors are used to sense the line and provide a change in voltage at comparator's second terminal. Then comparator compares both voltages and generates a digital signal at output. Here in this **line follower circuit** we have used two comparator for two sensors. LM 358 is used as comparator. LM358 has inbuilt two low noise Op-amps.

Control Section:

Arduino Pro Mini is used for controlling whole the process of line follower robot. The outputs of comparators are connected to digital pin number 2 and 3 of arduino. Arduino read these signals and send commands to driver circuit to drive line follower.

Driver section:

Driver section consists motor driver and two DC motors. Motor driver is used for driving motors because arduino does not supply enough voltage and current to motor. So we add a motor driver circuit to get enough voltage and current for motor. Arduino sends commands to this motor driver and then it drive motors.

If both sensors comes on black line, robot stops.

